

3E1614

Roll No. _____

[Total No. of Pages : 3]

3E1614

B.Tech. III Semester (Main/Back) Examination, Dec. - 2016
Applied Elect. & Inst. Engg.
3AI3 Circuit Analysis & Synthesis
EC, EI, EX, AI, BM

Time : 3 Hours

rtuonline.com

Maximum Marks : 80

Min. Passing Marks : 26


rtuonline.com

Instructions to Candidates:

Attempt any **five** questions, selecting one question from **each unit**. All questions carry equal marks. (Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.

Unit - I

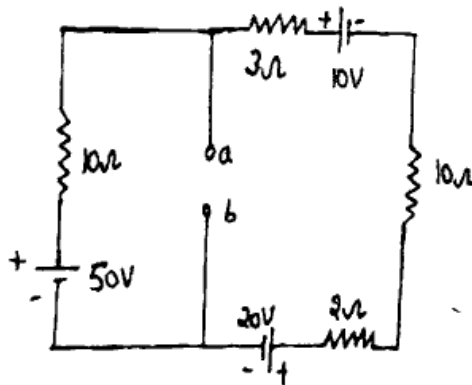
1. a) State and explain Thevenin's theorem with the help of suitable example. (8)
- b) Using superposition theorem, find the current through a link is to be connected between terminals a-b. Assume the link resistance to be zero.



(8)

OR

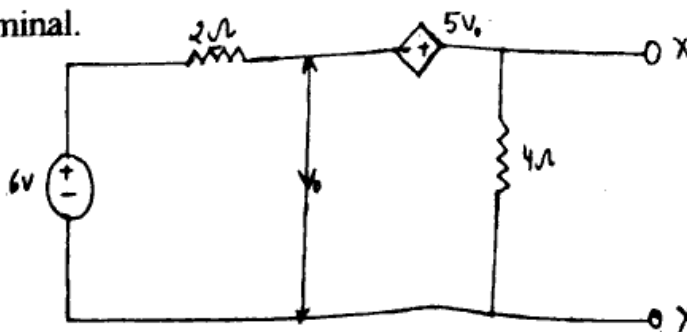1. a) State and prove maximum power transfer theorem. (8)
- b) Find the Norton's equivalent of the circuit shown in figure at the left of X-Y terminal. (8)




(1)

[Contd....

Unit - II

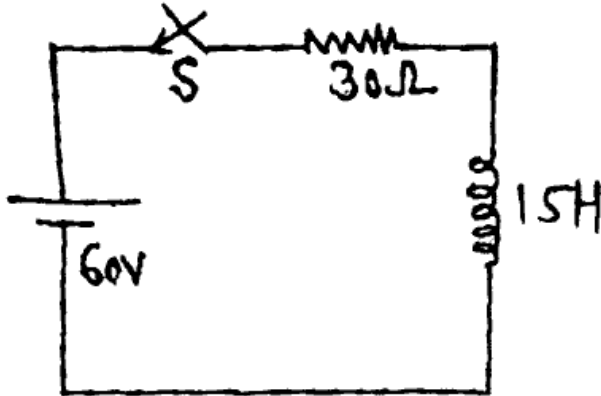2. a) A series RL circuit with $R = 30\Omega$ and $L = 15\text{ H}$ has a constant voltage $V = 60\text{ V}$ applied at $t = 0$ as shown in fig. Determine the current i , the voltage across resistor and the voltage across the inductor. (8)




- b) Explain different types of functions used in transient analysis. (8)

OR

2. a) Find the transient responses of :
 a) Series R-L
 b) Series R-C circuit having sinusoidal excitation (8)
 b) The step voltage applied to a series R-L circuit is 36 V with $R = 15\Omega$. Determine the value of inductance L required to make the current of 1.0 A at $250\ \mu\text{ sec}$. Assume the initial current is zero. (8)

Unit - III

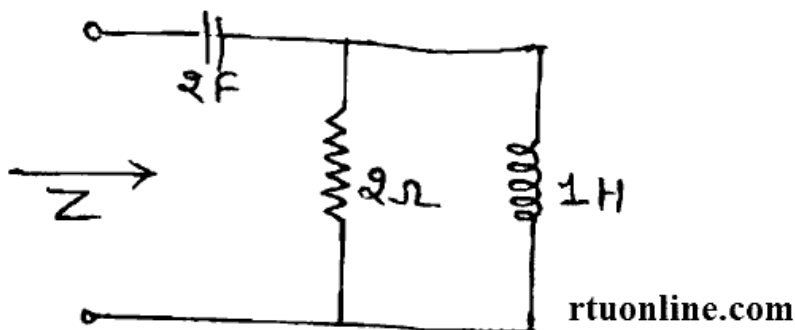3. a) Find $Z(s)$ for the following network. (8)



- b) Explain the relationship between pole position and stability. (8)

OR


3. a) Obtain the pale zero diagram of the given function and obtain the time domain response.

$$I(S) = \frac{2S}{(S+1)(S^2 + 2S + 4)} \quad (8)$$

- b) Check whether the following polynomial $P(S) = S^4 + S^3 + 2S^2 + 2S + 3$ is stable or not comment on your findings. rtuonline.com (8)

Unit - IV

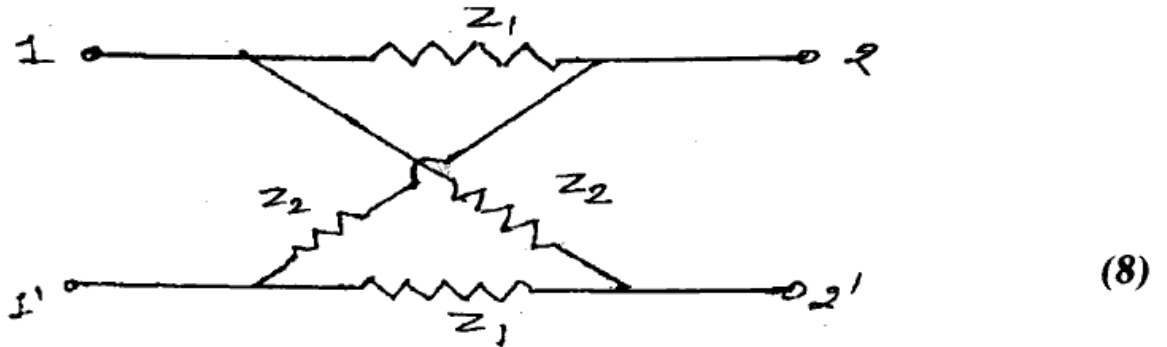
4. a) For the lattice two port network of fig. Find the image impedance and the image transfer constant.



- b) Derive Z-parameters in terms of hybrid parameters. (8)

OR

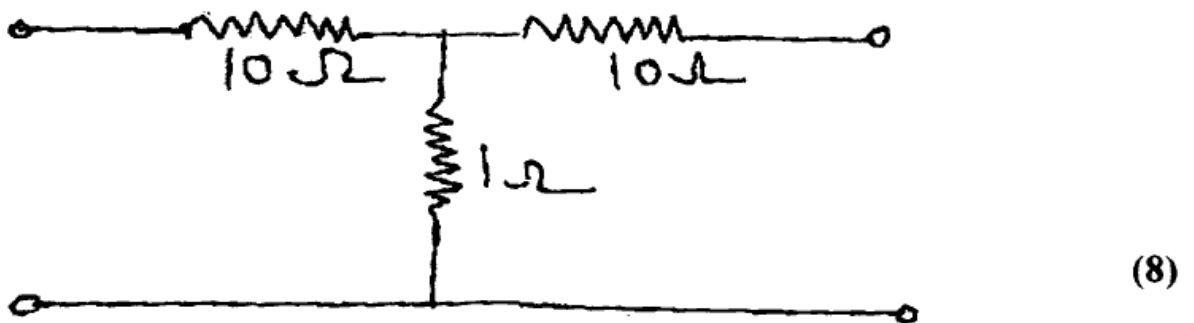4. a) Derive the condition for reciprocity and symmetry in case of ABCD parameters. (8)
- b) Two identical T section, as one shown in fig. are connected in cascade. Determine the Z-parameters of the combination.



Unit - V rtuonline.com

5. An impedance is given by $Z(s) = \frac{8(S^2 + 1)(S^2 + 3)}{5(S^2 + 2)(S^2 + 4)}$ Realise the network in Foster - I, II and cauer - I, II form. (16)

OR

5. Realise the function $z(s) = \frac{s(s^2 + 4)}{2(s^2 + 1)(s^2 + 9)}$ in both the cauer and foster forms of LC networks. (16)

rtuonline.com



(3)