

(c) A register contains 2's complement 10010110. What will be the contain of register if it is divided by 2.

4

OR

1 (a) Consider the signed binary number are $A = 01000110$ and $B = 11010011$ where B is in 2's complement form. Find the value of following Mathematical expression :

- (i) $A + B$
- (ii) $A - B$
- (iii) $B - A$
- (iv) $-A - B$

8

(b) Why the gray code is also known as reflected code ? Write a brief note on gray code and its applications.

8

UNIT - II

2 (a) What do you understand by following properties of logic family :

- (i) Fan out
- (ii) Figure of merit
- (iii) Noise margin
- (iv) Current mode logic.

8

- (b) Find the output boolean function (Y) in terms of A and B as shown in Fig. 1.

 


Fig. 1

OR

- 2 ✓ (a) A boolean function is implemented using NMOS logic family and shown in Fig. 2. How the output Y can be made 0 if C and D both values are 0. Also find implemented boolean function.

 


Fig. 2

- (b) State the advantage of using totem pole output type TTL, over open collector output TTL. Also explain the tristate output logic type TTL.

8

UNIT - III

- 3/ (a) Simplify the following boolean function using tabulation method :

$$F = \sum m(0, 1, 2, 8, 10, 11, 14, 15) \cdot d(9, 12).$$

10

- (b) Simplify the following boolean function using K-map :

$$Y = (A + B)(A + \bar{C})(\bar{A} + \bar{B})(\bar{A} + C).$$

6

OR

- 3 (a) The logic gate G_1 and G_2 as shown in Fig. 3 have propagation delay of 10 ns and 20 ns respectively. If input v_i makes an abrupt change from logic-0 to logic-1 at time $t = t_0$, then draw output waveform (V_0).

ns → nano second.

 


Fig. 3

8

- (b) Minimize the following boolean function using K-map :

$$f(a, b, c, d) = \sum m(0, 1, 2, 8, 9) \cdot d(4, 10, 12)$$

8

UNIT - IV

- 4 (a) How many 3 : 8 line decoder with enable input are required to construct 6 : 64 line decoder without using any other logic ? Draw its block diagram also. 8
- (b) Find the boolean function implemented by 4 : 1 mux as shown in Fig. 4.

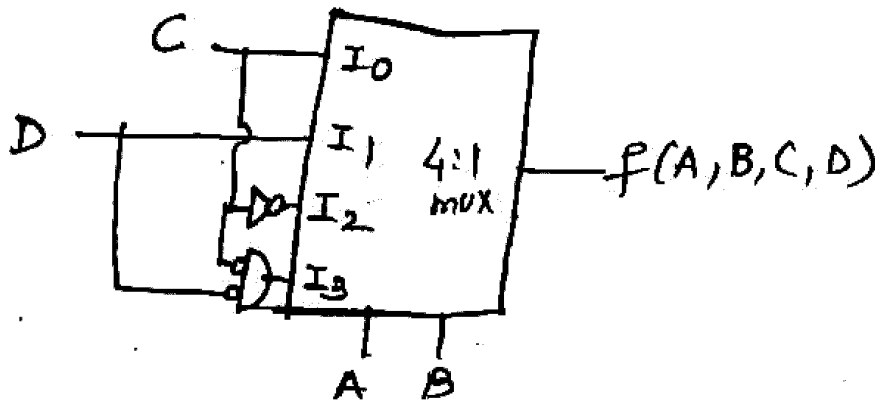


Fig. 4

OR

- 4 (a) Implement a full subtractor using two 4 : 1 multiplexer. 8

- (b) Find the output of following decoder circuit as shown in Fig. 5. 8

 


Fig. 5

(c) Find the output of 4:1 multiplexer as shown in Fig. 6.

 


Fig. 6

UNIT - V

- 5 (a) State the difference between latch and flip flop. 4
- (b) Explain the truth table, circuit-diagram and working of universal flip flop. 4
- (c) What are the counting states (Q_1, Q_0) for the circuit using D - flip flop as shown in Fig. 7 ?

 


Fig. 7

Assume initial state (Q_1, Q_0) is 00.

OR

5 / (a) Explain the procedure for conversion of JK flip flop to RS flip flop.

5

(b) What is race around condition ? How it can be avoided ?

5

(c) Design a binary counter with following binary sequence using D - flip flop :
0, 1, 3, 2, 6, 4, 5, 7 and repeat.

6