

3E1653

3E1653

B. Tech. III - Sem. (Main / Back) Exam., Dec. - 2018
Electronic Instrumentation & Control Engineering
3EI3A Digital Electronics
EE, EX, EC, EI, CS, IT, AI

Time: 3 Hours

Maximum Marks: 80
Min. Passing Marks: 26

Instructions to Candidates:

Attempt any five questions, selecting one question from each unit. All questions carry equal marks. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly.

Units of quantities used/calculated must be stated clearly.

Use of following supporting material is permitted during examination.
(Mentioned in form No. 205)

1. NIL

2. NIL

UNIT-I

Q.1 (a) Find the unknown number –

[4×2=8]

(i) $(123)_{10} + (?)_{10} = (BA)_{16}$

(ii) $(11000)_2 + (143)_8 = (?)_{10}$


(iii) $(1A)_{16} + (342)_8 = ()_4$

(iv) $(?)_2 + (102)_8 = (420)_{16}$


(b) Convert following –

[2+2+4=8]


(i)

 

(ii)

 

(iii)

 

OR

Q.1 (a) Convert following - [4×2=8]


- (i) (1010) gray code → into excess - 3 code
- (ii) $(1.204)_{10} = ()_2$
- (iii) $(0.001)_2 + (1000)_8 = ()_{16}$
- (iv) $(242)_8 + (2.42)_8 = ()_2$

(b) Define following - [4×2=8]

- (i) Sign representation in Binary no.
- (ii) Negative logic
- (iii) Universal logic
- (iv) Fixed point representation

UNIT- II

 Q.2 (a) Calculate the logic level for high and low output in logic circuit (fig - 2 (i)) [8]



Assume the diode drop is 0.7 volt and the standard input logic level are

0 → 0 volt


1 → 9 volt

Also explain the logic performed by this circuit.

(b) Explain the logic performed by the MOSFET circuit Fig – 2 (ii). Also discuss about the high and low voltage levels in this logic under following conditions- [8]

(i) $R_D = 100 \Omega$ (Very Small)

(ii) $R_D = 100 M\Omega$ (Very High)

 

OR

Q.2 (a) What is HTL? Design a 2 – input AND HTL gate to achieve noise margin of 2.5 volt. [8]

(b) Draw the circuit diagram of I²L logic and explain its working. Where these logics are preferable? http://www.rtuonline.com [8]

UNIT- III

Q.3 (a) Draw K – map for following and find the minimized logic expression for output. [4+4=8]

(i) $y = \sum m (2, 5, 6, 8, 12, 13, 14) + d (3, 9)$

(ii) $y = \pi m (0, 1, 2, 7) + d (4, 5)$

(b) Minimize following – [4+4=8]

(i) $y = \overline{(A + B)(\bar{C} + D)} + \overline{A\bar{B}C}$ using simplification.

(ii) $y = \sum (0, 1, 2, 6, 7)$ using Quine – McCluskey method.

OR

Q.3 (a) In a 4 – variable K – map there are following groups formed. [8]

(i) 2 – Quad (four entries)

(ii) 2 – two entries group.

Write all possible minimized logic expressions for it.

(b) Express following in -

[2×2=4]

(i) $y = AB (\bar{C} + D)$ in POS

(ii) $y = (A + B) + \bar{C}D$ in SOP

(c) Discuss the role of don't care conditions in minimization.

[4]

UNIT- IV

Q.4 (a) Draw the Block diagram of a serial 4 bit adder and calculates its total time taken in addition in terms of clocks. [8]

(b) Implement a 16×1 mux in terms of 2×1 mux. Also estimate its total delay from input to output. Compare this delay with a direct implementation of 16×1 Mux. [8]

OR

Q.4 (a) Design an octal to binary converter. [8]

(b) Draw the circuit diagram of a 2 bit multiplier. [8]


UNIT- V

Q.5 (a) Draw Synchronous Modulo - 7 Counter and explain its working. [8]

(b) Design a counter that count from 0 - 12 but skip 6, 7 and 9. [8]

OR

 Q.5 (a) Draw the logic circuit for the state diagram given in fig - 5 [8]



(b) Draw state diagram of a JK and D - FF. Also discuss their inter conversion. [8]