

<b>3E1641</b>	Roll No. _____	Total No. of Pages : <b>7</b>
	<b>3E1641</b>	
<b>B. Tech. (Sem. III) (Main/Back) Examination, December - 2017</b>		
<b>Applied Elect. &amp; Inst. Engg.</b>		
<b>3AI2 Electronic Devices &amp; Circuits (EC, EIC, EE, EX, AI, BM)</b>		

Time : 3 Hours

Maximum Marks : 80

Min. Passing Marks : 26

*Attempt any five questions, selecting one question from each unit.  
All Questions carry equal marks. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly. Units of quantities used / calculated must be stated clearly.*

*Use of following supporting material is permitted during examination.  
(Mentioned in form No. 205)*

1. \_\_\_\_\_ Nil                      2. \_\_\_\_\_ Nil

### UNIT - I

- 1 (a) What is the position of the fermi level in an intrinsic semiconductor?  
How does its position change when :
- (i) donor and
  - (ii) acceptors are added to the semiconductor ?

5

3E1641 ]

1

[ P.T.O.

- (b) A sample of Ge is doped to the extent of  $10^{14}$  donor atoms/cm<sup>3</sup> and  $5 \times 10^{13}$  acceptor atoms/cm<sup>3</sup> at 300 K, the resistivity of intrinsic Ge is  $60 \Omega - cm$ . If the applied electric field is 2 V/cm, find the total conduction current density. Assume  $\mu_p/\mu_n = 1/2$  and  $n_i = 2.5 \times 10^{13} / cm^3$  at 300 K.

8

- (c) What is mass action for the carrier concentration ?

3

OR

- 1 (a) What are "Hall effect" and "Hall field" ? Explain briefly the physical origin of the Hall effect.


8

- (b) A rectangular semiconductor specimen, 2 mm wide and 1 mm thick, gives a Hall coefficient of  $10^{-2} m^3/c$ . When a current of 1 mA is passed through the sample, a Hall voltage of 1 mV is developed find the magnetic field and the Hall field. <http://www.rtuonline.com>

8
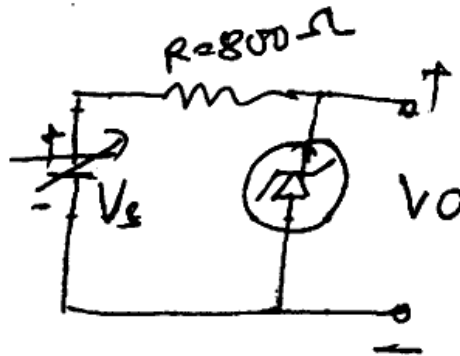
## UNIT - II

- 2 (a) In the circuit of figure the Zener diode is non ideal, having a knee voltage  $V_{z0} = 9V$  and a dynamic resistance  $r_z = 5\Omega$ . If the supply voltage  $V_s$  varies from 15 to 30V, determine the range of variation of the output voltage  $V_o$ , also comment on the result.



8

- (b) (i) What is unijunction transistor ? Give the equivalent circuit.  
(ii) Draw and explain its current voltage characteristics.

8

OR

- 2 (a) The voltage waveform  $v_i$  of Figure (a) is applied to the input of the circuit of Figure (b). Show the output voltage  $V_o$  waveform and mark the voltage levels.

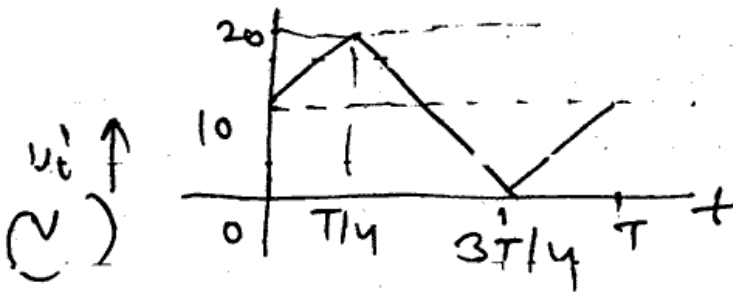


Figure (a)

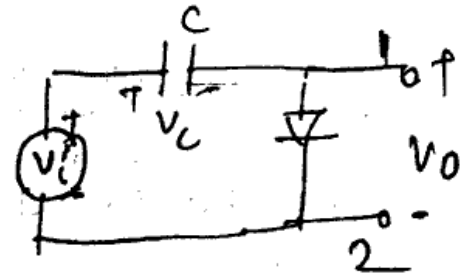


Figure (b)

Find the PIV of the diode, assumed to be ideal.

8

- (b) Draw the circuit diagram of a fullwave voltage doubler and explain its operation, how can we construct a voltage tripler ?

8

http://www.rtuonline.com

UNIT - III

- 3 (a) Draw the circuit diagram of an emitter follower. Why it is called an emitter follower? Obtain expression for the current gain, input resistance voltage gain and output resistance.

12

- (b) A transistor is operating in the CE mode calculate  $V_{CE}$  if  $\beta = 125$ ,  $V_{BE} = 0.6 V$ .


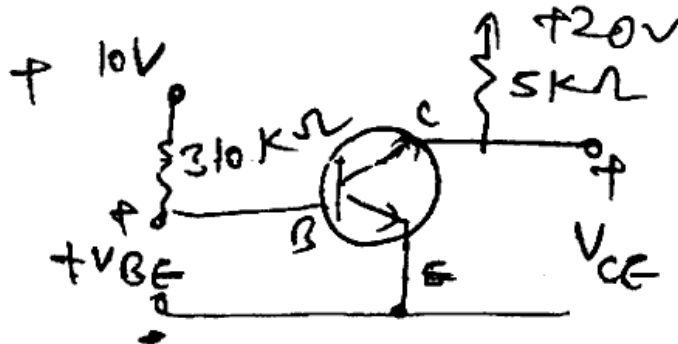


Figure 3(b)

4

OR

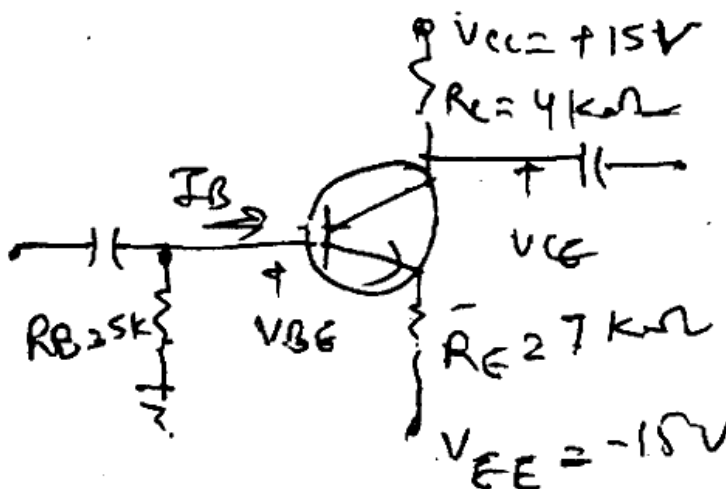- 3 (a) In the circuit of figure shown below,  $\beta = 99$  and  $V_{BE} = 0.7V$ . Calculate the quiescent values of  $I_B$ ,  $I_C$ ,  $I_E$  and  $V_{CE}$ . If  $\beta$  is increases by 20% what is the corresponding change in  $I_C$ ?



$R_B = 5k\Omega$ ,  $R_E = 7k\Omega$   
 $R_C = 4k\Omega$   
 $V_{CC} = +15V$   
 $V_{EE} = -15V$

9

- (b) Draw and label the low frequency h-equivalent of CE amplifier and obtain voltage gain.

7

### UNIT - IV

- 4 (a) Derive an expression for the small signal voltage gain of a common source FET amplifier.

8

- (b) A n-channel JFET has  $I_{DSS} = 12$  mA and Pinch off voltage  $V_p = -4$ V. Find the drain current for  $V_{GS} = -2$ V. If the transconductance  $g_{mo}$  of a JFET with the same  $I_{DSS}$  at  $V_{GS} = 0$  is 4 millimho, find the pinch off voltage.


8

OR

- 4 (a) Sketch the structure of n-channel depletion type MOSFET. Explain how the depletion region is produced in the channel. Can a depletion MOSFET work in the enhancement mode ?

8

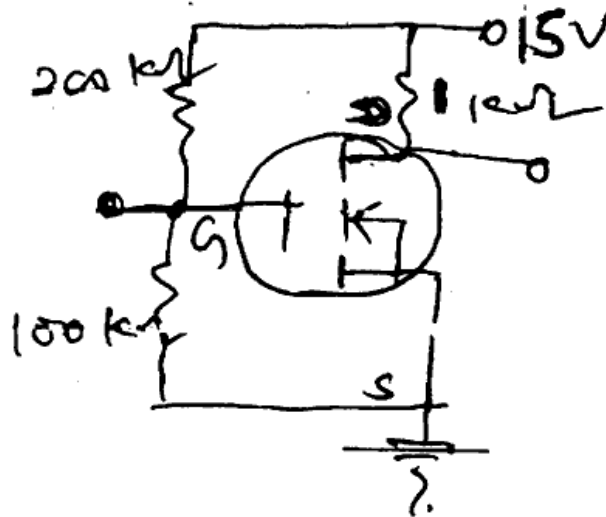- (b) An n-channel enhancement mode MOSFET, biased as shown in Fig. operates in the active region. The given parameters are  $V_T = 2V$  and  $K = 0.5 \text{ mA/V}^2$ . Calculate  $I_D$ ,  $V_{GS}$  and  $V_{DS}$  verify that the operation is indeed in the active region.



8

UNIT - V

- 5 (a) An RC coupled amplifier employs two identical transistors, each having  $h_{fe} = 100$ ,  $h_{ie} = 2k\Omega$  and  $C_{of} = 2PF$ . The coupling capacitor has a capacitance  $C = 0.4 \mu F$ . The load resistance for each transistor is  $R_L = 8 k\Omega$ . The wiring capacitance  $C_W = 10 PF$ , calculate the lower and upper half power frequencies.
- (b) Obtain an expression for the voltage gain of an R-C coupled amplifier in the mid, low and high frequency ranges.

8

8

OR

5 (a) Draw the circuit diagram of a common source n channel JFET amplifier.  
Discuss its small signal operation.

10

(b) What is the Darlington connection, compare between an emitter follower and a darlington pair ?

6