

3E1642

Roll No. _

3E1642

B. Tech. III - Sem. (Back) Exam., Dec. - 2018

Electrical Engineering
3EE2A Circuit Analysis - I

Time: 3 Hours

Maximum Marks: 80
Min. Passing Marks: 24

Instructions to Candidates:

Attempt any five questions, selecting one question from each unit. All questions carry equal marks. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly.

Units of quantities used/calculated must be stated clearly.

Use of following supporting material is permitted during examination.
(Mentioned in form No. 205)


1. NIL

2. NIL


UNIT-I

Q.1 (a) Develop the graph of the network shown in the figure given below. Select the tree and write the- [8]

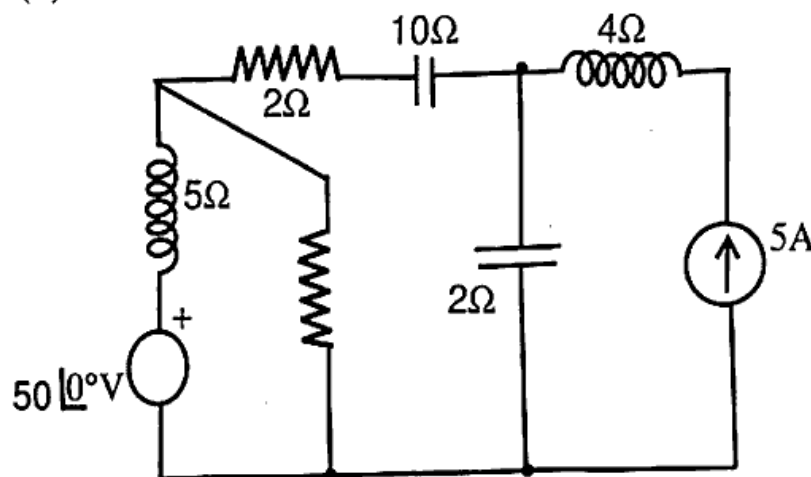- (i) Tie Set Matrix
- (ii) Cut - set Matrix



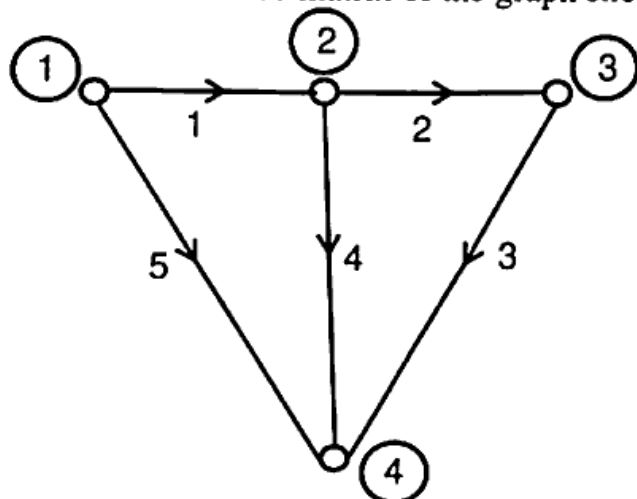- (b) Obtain the incidence matrix of the graph shown as given below. [8]



OR


- Q.1 (a) Explain the variation of resistance, inductive and capacitive reactance with frequency. [8]
(b) Write a short note on parallel RLC circuit resonance. [8]

UNIT- II

- Q.2 (a) State Thevenin's theorem. Also write the steps for solving a network using Thevenin's theorem. [8]
(b) Explain Reciprocity theorem with the steps for solving a network. [8]

OR

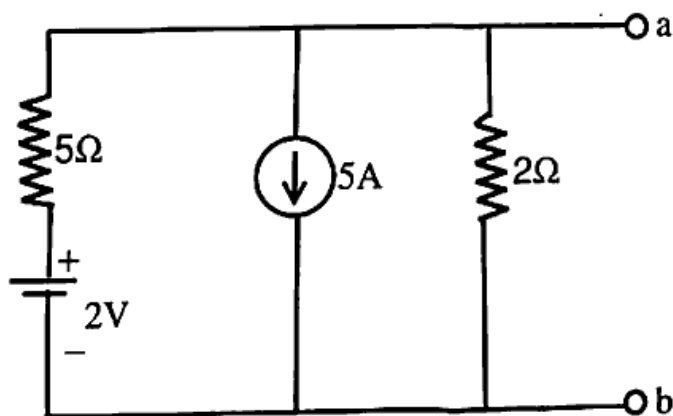- Q.2 (a) Explain the Compensation theorem with its limitation. [8]
(b) Find the Norton's equivalent circuit across a-b for the network shown as in given figure. [8]



UNIT- III


- Q.3 (a) What is the relationship between line and phase voltages and currents in a star connection? [8]
- (b) Write short note on- [4×2=8]
- (i) Power factor
 - (ii) Apparent power
 - (iii) Reactive power
 - (iv) Power Triangle

OR

- Q.3 (a) A 3 phase load has a resistance of 10Ω in each phase and is connected in (i) Star and (ii) Delta against a 400V three phase supply. Compare the power consumed in both the cases. <http://www.rtuonline.com> [8]
- (b) A Voltage $V(t) = 150 \sin 10^3 t$ is applied a series RLC Circuit where, $R = 40\Omega$, $L = 0.13H$, $C = 10\mu F$. [8]
- Find-
- (i) The power supplied by the source
 - (ii) The reactive power supplied by the source
 - (iii) The reactive power of the capacitor
 - (iv) The reactive power of the inductor

UNIT- IV \propto

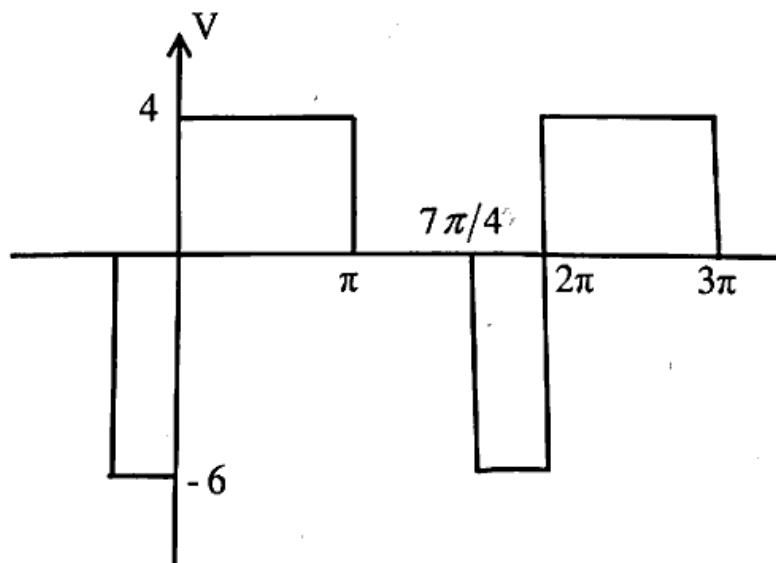
- Q.4 (a) Find a and b coefficient of Fourier series of the given waveform. [16]



OR

Q.4 (a) Obtain the exponential Fourier series of the waveform given as.

[8]

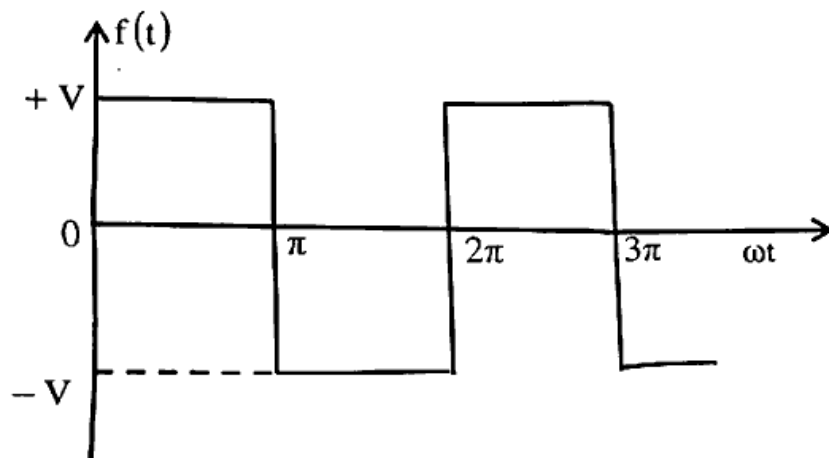

(b) Write short note on Symmetry in Fourier series.

[8]

UNIT- V

Q.5 (a) Explain the step response of R-L network.

[8]

(b) Explain the initial value and final value theorem.

[8]

OR

Q.5 (a) An impulse function is given by $\delta(t - t_1)$. Obtain its Laplace transform.

[8]

(b) A function, in Laplace domain is given by-

[8]

$$F(s) = \frac{2}{s} - \frac{1}{s+3}$$

Obtain its value by Final value theorem in t domain.

<http://www.rtuonline.com>

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से

<http://www.rtuonline.com>