

**Total No. of Pages : 3**

**4E2109**

**Electrical Engg.**

## 4EE1(O) Power Electronics - II

**Maximum Marks : 80**

**Min. Passing Marks : 26**

*Attempt any five questions, selecting one question from each unit. All Questions carry equal marks. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly.*

Units of quantities used / calculated must be stated clearly.

*Use of following supporting material is permitted during examination.*

(Mentioned in form No. 205)

1. NIL

## UNIT - I

- 1 (a) What are the advantages of negative feedback in amplifiers ? Derive the input impedance  $R_{if}$  of a voltage series and current shunt feedback amplifier.
- (b) An amplifier has a voltage gain of 4000. Its input impedance is 2K and output impedance is 60 K. Calculate the voltage gain, input and output impedance of the circuit if 5% of the feedback is fed in the form of series negative voltage feedback.

**OR**

- 1 (a) Explain the concept of feedback with the help of block schematic of a signal loop feedback amplifier. Derive expression for the transfer gain with feedback.

- (b) Draw the circuit diagram of a two stage amplifier employing current shunt feedback and obtain the expression of its gain with feedback.

## UNIT - II

- 2 (a) What is the Barkhausen criterion for the feedback oscillators ? Explain the principle of working of Colpitts oscillator.  
(b) What type of feedback is employed in oscillators ? Explain how amplitude and frequency stability are improved in an oscillators.

### OR

- 2 (a) Why are the RC oscillators preferred for the generation of low frequencies ? Draw a neat circuit diagram of a phase shift oscillator using BJT. Derive an expression for its frequency of oscillation.  
(b) In a Hartley oscillator,  $L_1 = 15 \text{ mH}$  and  $C = \text{pF}$ . Calculate  $L_2$  for a frequency of  $168 \text{ kHz}$ . The mutual inductance between  $L_1$  and  $L_2$  is  $5 \text{ } \mu\text{H}$ . Also find the required gain of the transistor to be used for the oscillator.

## UNIT - III

- 3 (a) What is the mean by CMMR ? Derive the expression for CMMR in an emitter coupled differential amplifier.  
(b) How a differentiator circuit can be designed using an ideal operation amplifier ? Explain.

### OR

- 3 (a) Draw and explain logarithmic and antilog amplifier by using operation amplifier. Derive the expression of logarithmic amplifier.  
(b) Explain the slew rate. For an operation amplifier having a slew rate of  $3 \text{ v}/\mu\text{sec}$ . What is the maximum closed loop voltage gain that can be used when the input signal varied by  $0.4 \text{ v}$  in  $12 \text{ } \mu\text{sec}$  ?

**UNIT - IV**

- 4 (a) Define the following term of D/A conversion :
- (1) Resolution
  - (2) Accuracy
  - (3) Monotonicity
  - (4) Conversion time.
- (b) Draw and explain the series emitter follower regulated power supply circuit.

**OR**

- 4 (a) Draw and explain the functional diagram of IC 555 timer and explain an application with the help of circuit diagram.
- (b) Write short note on three terminal monolithic regulator.

**UNIT - V**

- 5 (a) Define the conversion efficiency. Compare maximum efficiency of a series fed and transformer coupled class A signal transistor power stage.
- (b) Show that optimum conversion efficiency possible in class B push pull amplifier is 78.5% and also explain the main drawback of class B configuration in power amplifier.

**OR**

- 5 (a) Write short note on complementary symmetry power amplifiers.
- (b) Prove that in class A amplifier if distortion is 10 percent power gain to the load is increased by 1 percent
-